

Candidate seat No: _____

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

B. Tech. (CE/CS/IT/EC) Sem-I Theory Examination

(February 2022)

Course: EE 145 Basics of Electronics & Electrical Engineering


Maximum Marks: 70


Date: 16/02/2022 (Wednesday)


Time: 10:00 a.m. to 01:00 p.m.

Instructions:

- (i) Attempt *all* the questions.
- (ii) Figures to the right indicate *full* marks.
- (iii) Make suitable assumptions and draw neat figures wherever if required.
- (iv) Paper Uploading Time- 40 Minutes Extra for uploading the paper

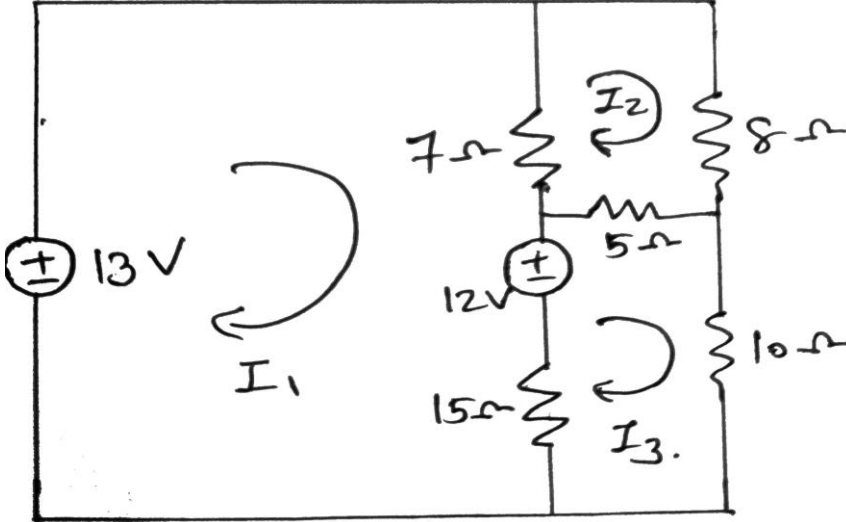Q-2	Answer the Following Questions. (Any Five)	[25]
A	<p>A copper coil has a resistance of 25 ohm at 31 degree Celsius and 37 ohms at 55 degree Celsius, calculate:-</p> <ul style="list-style-type: none">1). Temperature co-efficient of resistance at 0 degree Celsius2). Resistance of coil at 0 degree Celsius3). Temperature co-efficient of resistance at 85 degree Celsius4). Resistance of coil at 60 degree Celsius	
B	<p>Determine the mesh currents I_1, I_2 and I_3 for the network shown in fig a. by using KVL.</p>  <p style="text-align: right;">fig a.</p>	

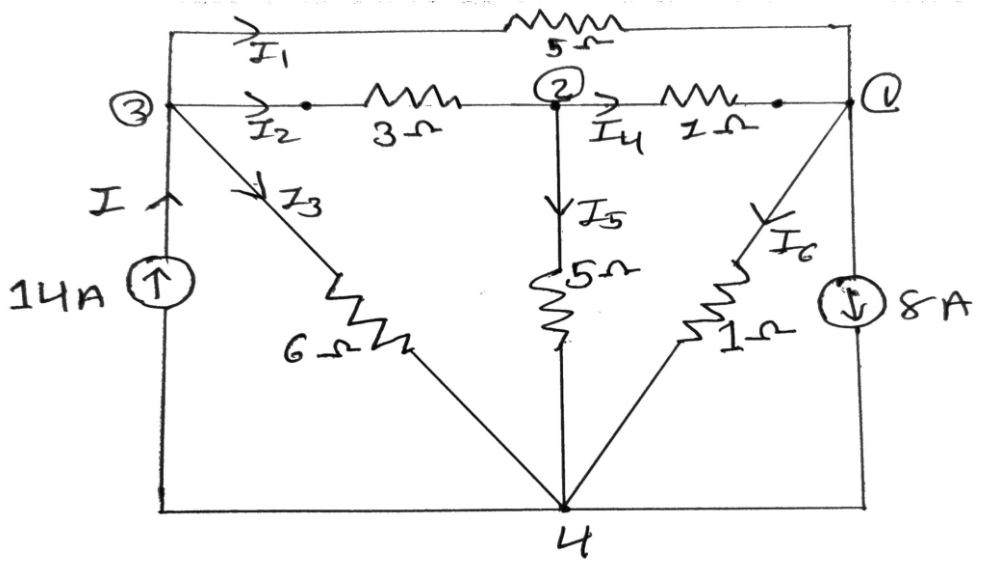C	<p>Using nodal analysis calculate the currents in the various resistors of the circuit shown in fig b.</p>  <p style="text-align: right;">fig b.</p>	
D	<p>A parallel plate capacitor has plates of area 5 m^2 spaced by the three slabs of different dielectrics. The relative permittivity are 4, 7 and 11 and the thickness 0.8, 1.3 and 1.7 mm respectively. Calculate the combined capacitance and the dielectric stress in each material. When the applied voltage is 970 V.</p>	
E	<p>An alternating emf is represented by $e=141.4*\sin 377t$ Calculate (i) Maximum value (ii) Frequency (iii) Time period (iv) Instantaneous value of voltage when t is 3 milliseconds.</p>	
F	<p>A series LC circuit has an inductance of $200\mu\text{H}$, A Capacitance of 300pF and Q of 60. Determine i) Resonance frequency ii). Bandwidth iii). Upper and lower cut-off frequency</p>	

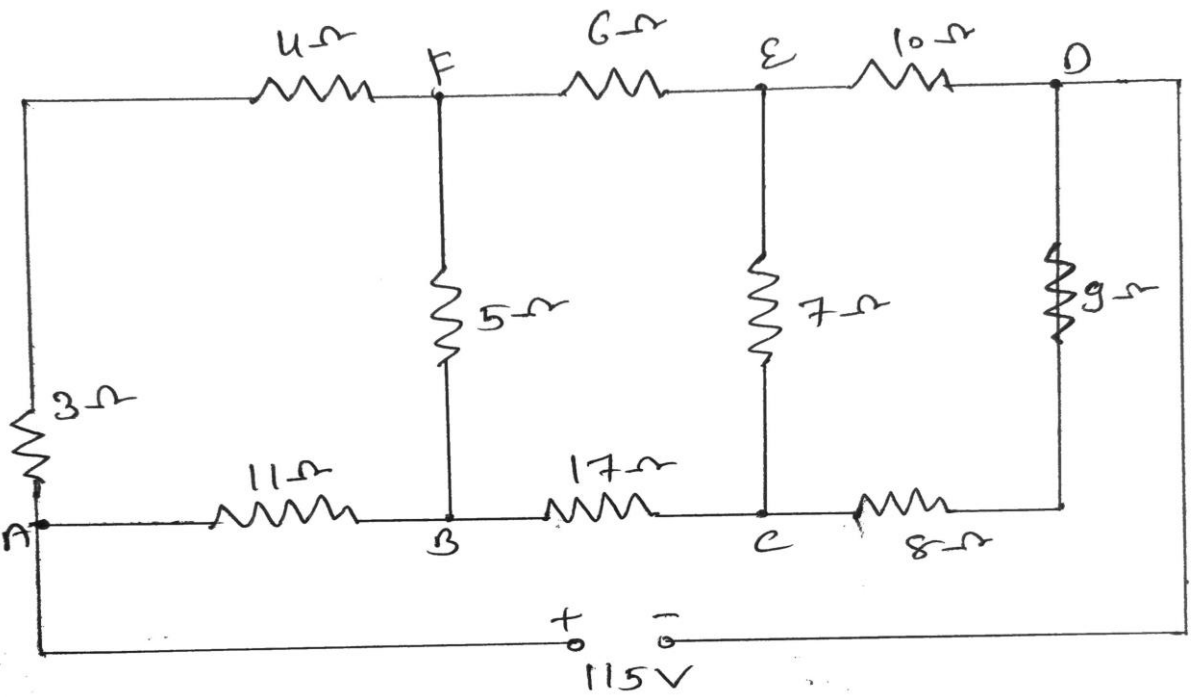G	<p>Determine the current in the $17\ \Omega$ resistor in the network shown in fig c. using the delta-star transformation.</p>  <p style="text-align: center;">fig c</p>	
Q-3	Answer the Following Questions. (Any Five)	[25]
A	<p>Give the definition</p> <ol style="list-style-type: none"> 1. Potential difference 2. Active & passive element 3. Loop & Mesh 4. Conductance & conductivity 5. Electrical energy 	
B	Explain and derive the charging equation of capacitor voltage with necessary diagrams.	
C	Derive the equation of resistance for star to delta transformation.	
D	Comparison between electric and magnetic circuit. (Minimum 10 points)	
E	Explain basic principle of Generation of Alternating voltage and derive equation of alternating Voltage $e = E_m \sin \omega t$ for single phase circuit.	
F	Explain series R-L circuit with phasors diagram and waveform. Also explain power factor, active power, reactive power, apparent power.	
G	Explain in detail the Voltage and current relation in 3-phase delta connected system.	
H	Explain common emitter connection with current amplification factor and expression for output current and also explain Input and output characteristics of Common Emitter connection.	
