

CHAPTER 6

SEQUENTIAL LOGIC


INTRODUCTION

Combinational Circuits: A circuit whose output, at any instant of time are dependent upon the input present at that time.

i.e. Half Adder, Full Adder

Sequential Circuits: A circuit whose output depends not only on the present inputs but also on the past history of inputs.

i.e. Flipflop

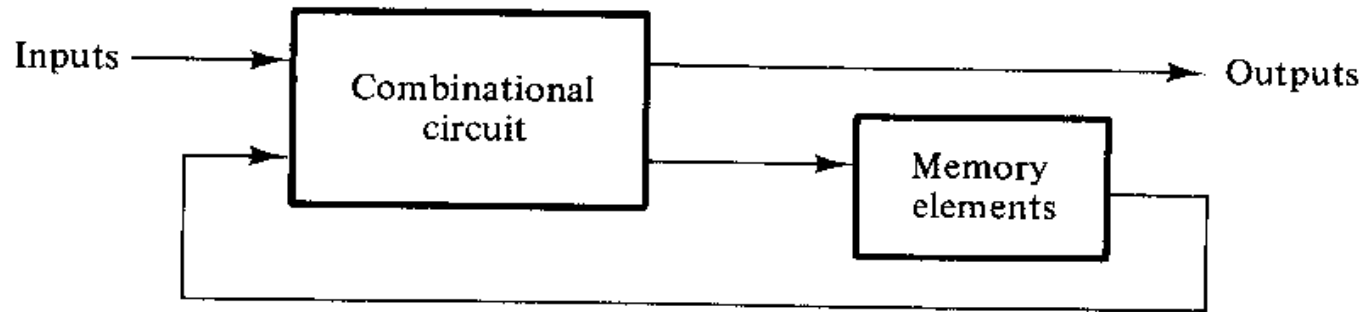

- The memory element is devices capable of storing binary information within them.
- The input is provided by external input.
- These inputs, together with the present state of the memory elements, determine the binary value at the Output terminal as well as the condition for changing the state in the memory elements.

Types of Sequential Circuits:

Synchronous Sequential Circuit: is a system whose behavior can be defined from the knowledge of its signals at discrete instant of time.


Asynchronous Sequential Circuit: is a system whose behavior depends upon the order in which its input signals change and can be affected at any instant of time.

Clocked Sequential Circuit: Synchronous Sequential Circuits that use clock pulses in the inputs of memory elements are called Clocked Sequential Circuit.

FlipFlops:

- The memory elements used in sequential circuits are called as FlipFlops.
- These circuits are binary cells capable of storing **one bit** of information.
- A FlipFlop has **two outputs**, one for the **normal value** and one for the **complement value** of the bit stored in it.

 
- FlipFlop circuit can be constructed from two NAND gates or two NOR gates.
- The cross-coupled connection from the output of one gate to the input of the other gate constitutes a feedback path.
- Each FlipFlop has two outputs, Q and Q' , and two inputs SET and RESET.
- This type of FlipFlop is called DIRECT COUPLED RS FLIPFLOPS or SR LATCH.



(a) Logic diagram

S	R	Q	Q'	
1	0	1	0	
0	0	1	0	(after $S = 1, R = 0$)
0	1	0	1	
0	0	0	1	(after $S = 0, R = 1$)
1	1	0	0	


(b) Truth table

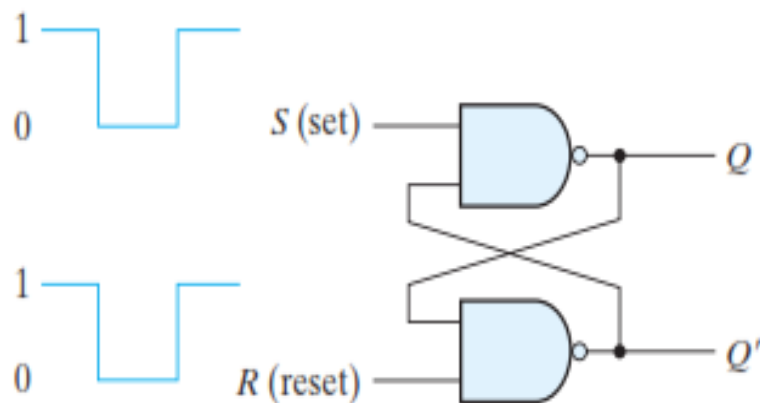

(a) Logic diagram

S	R	Q	Q'
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$)
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$)
0	0	1	1 (forbidden)

(b) Function table

 


(a) Logic diagram

CP	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

(b) Function table

SR latch with control input

D FLIP-FLOP

 


(a) Logic diagram

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

(b) Function table


JK FLIP-FLOP

 

Q	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Characteristic table



T FLIP FLOP

 


Q	T	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

Characteristic table


TRIGGERING OF FLIP FLOPS

  


MASTER SLAVE FLIP-FLOP

 

MASTER SLAVE FLIP-FLOP

 


EDGE-TRIGGERED FLIP-FLOP

 


- $CP = 0 \Rightarrow S \ \& \ R = 1 \Rightarrow$ STEADY STATE OUTPUT
- $D = 0 \ \& \ CP = 1 \Rightarrow S = 1, R = 0 \Rightarrow Q = 0$
- $D = 1 \ \& \ CP = 1 \Rightarrow S = 0, R = 1 \Rightarrow Q = 1$


Graphic Symbols

 


(a) RS

 

(b) JK

 


(c) D

 

(d) T

Analysis of Clocked Sequential Circuit

 

$$A(t + 1) = Ax + Bx$$

$$B(t + 1) = A'x$$

$$y = (A + B)x'$$

State - Table

State Table for the Circuit


Present State		Input	Next State		Output
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

State - Table

Second Form of the State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
	AB	AB	y	y
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0

State Diagram

 


Flip – Flop Input Function

$$JA = BC'x + B'Cx'$$

$$KA = B + y$$

$$y = (A + B)x'$$

 

Flip – Flop Characteristic Tables

Flip-Flop Characteristic Tables

<i>JK</i> Flip-Flop			
<i>J</i>	<i>K</i>	$Q(t + 1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement


<i>D</i> Flip-Flop		
<i>D</i>	$Q(t + 1)$	
0	0	Reset
1	1	Set

<i>RS</i> Flip-Flop			
<i>S</i>	<i>R</i>	$Q(t + 1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Unpredictable

<i>T</i> Flip-Flop		
<i>T</i>	$Q(t + 1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

Sequential Circuit With J-K Flip-Flop

 
$$\begin{array}{ll} JA = B & JB = x' \\ KA = Bx' & KB = A'x + Ax' = A \oplus x \end{array}$$



[illegible]

1. $\frac{1}{2} \log \frac{1}{2}$ 2. $\frac{1}{2} \log \frac{1}{2}$ 3. $\frac{1}{2} \log \frac{1}{2}$ 4. $\frac{1}{2} \log \frac{1}{2}$ 5. $\frac{1}{2} \log \frac{1}{2}$ 6. $\frac{1}{2} \log \frac{1}{2}$ 7. $\frac{1}{2} \log \frac{1}{2}$ 8. $\frac{1}{2} \log \frac{1}{2}$ 9. $\frac{1}{2} \log \frac{1}{2}$ 10. $\frac{1}{2} \log \frac{1}{2}$

Sequential Circuit With J-K Flip-Flop

 

Mealy & Moore Models

- **Mealy Model**


- The outputs are functions of both the **Present state & Inputs**
- In figure 6.16, output Y is function of both input X & the present state of A & B
- The outputs may change if the inputs change during the clock pulse period.

Mealy & Moore Models

- **Moore Model**

- The outputs are a function of the **Present state only**
- In figure 6.19, the output is taken from flipflop and are a function of present state only
- The outputs of sequential circuit are synchronized with the clock because they depend on only flipflop outputs that are synchronized with the clock

State Reduction and Assignment

 

State Reduction and Assignment

State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f'	0	1
e	a	f	0	1
f	g'	f	0	1
g	a	f	0	1

State Reduction and Assignment

Reducing the State Table


Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1
<i>f</i>	<i>ge</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

State Reduction and Assignment

Reduced State Table

Present State	Next state		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1

State Reduction and Assignment

 

State Reduction and Assignment

Three Possible Binary State Assignments

State	Assignment 1	Assignment 2	Assignment 3
<i>a</i>	001	000	000
<i>b</i>	010	010	100
<i>c</i>	011	011	010
<i>d</i>	100	101	101
<i>e</i>	101	111	011

State Reduction and Assignment

Reduced State Table with Binary Assignment 1

Present state	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
001	001	010	0	0
010	011	100	0	0
011	001	100	0	0
100	101	100	0	1
101	001	100	0	1

Flip Flop Excitation Tables

Flip-Flop Excitation Tables

$Q(t)$	$Q(t + 1)$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

(a) RS

$Q(t)$	$Q(t + 1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

(b) JK

$Q(t)$	$Q(t + 1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

(c) D


$Q(t)$	$Q(t + 1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

(b) T

Design Procedure

1. The word description of the circuit behavior is stated. This may be accompanied by a state diagram, a timing diagram, or other pertinent information.
2. From the given information about the circuit, obtain the state table.
3. The number of states may be reduced by state-reduction methods if the sequential circuit can be characterized by input–output relationships independent of the number of states.
4. Assign binary values to each state if the state table obtained in step 2 or 3 contains letter symbols.
5. Determine the number of flip-flops needed and assign a letter symbol to each.
6. Choose the type of flip-flop to be used.
7. From the state table, derive the circuit excitation and output tables.
8. Using the map or any other simplification method, derive the circuit output functions and the flip-flop input functions.
9. Draw the logic diagram.

Circuit Design Using JK Flip Flop

 

Circuit Design Using JK Flip Flop

State Table

Present State		Next State			
		$x = 0$		$x = 1$	
		A	B	A	B
0	0	0	0	0	1
0	1	1	0	0	1
1	0	1	0	1	1
1	1	1	1	0	0

Circuit Design Using JK Flip Flop

Excitation Table

Inputs of Combinational Circuit					Outputs of Combinational Circuit			
Present State		Input	Next State		Flip-Flop Inputs			
<i>A</i>	<i>B</i>	<i>x</i>	<i>A</i>	<i>B</i>	<i>JA</i>	<i>KA</i>	<i>JB</i>	<i>KB</i>
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

Circuit Design Using JK Flip Flop

		Bx		B
A	00	01	11	10
0				1
1	X	X	X	X

x

$$JA = Bx'$$

X	X	X	X
		1	

$$KA = Bx$$


	1	X	X
	1	X	X

$$JB = x$$

X	X		1
X	X	1	

$$KB = (A \oplus x)'$$

Circuit Design Using JK Flip Flop

 

Circuit Design Using D Flip Flop

$$DA(A, B, x) = \Sigma (2, 4, 5, 6)$$


$$DB(A, B, x) = \Sigma (1, 3, 5, 6)$$

$$y(A, B, x) = \Sigma (1, 5)$$


State Table for Design with D Flip-Flops

<u>Present State</u>		<u>Input</u>	<u>Next State</u>		<u>Output</u>
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	<i>y</i>
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	0	0	0

Circuit Design Using D Flip Flop

 

Circuit Design Using D Flip Flop

 

Design With Unused States Using SR Flip Flop

State Table with Unused States

Present State			Input	Next State			Flip-Flop Inputs						Output
A	B	C		A	B	C	SA	RA	SB	RB	SC	RC	y
0	0	1	0	0	0	1	0	X	0	X	X	0	0
0	0	1	1	0	1	0	0	X	1	0	0	1	0
0	1	0	0	0	1	1	0	X	X	0	1	0	0
0	1	0	1	1	0	0	1	0	0	1	0	X	0
0	1	1	0	0	0	1	0	X	0	1	X	0	0
0	1	1	1	1	0	0	1	0	0	1	0	1	0
1	0	0	0	1	0	1	X	0	0	X	1	0	0
1	0	0	1	1	0	0	X	0	0	X	0	X	1
1	0	1	0	0	0	1	0	1	0	X	X	0	0
1	0	1	1	1	0	0	X	0	0	X	0	1	1

Design With Unused States Using SR Flip Flop

AB		C			
		00	01	11	10
A	00	X	X		
	01		1	1	
	11	X	X	X	X
	10	X	X	X	

$SA = Bx$

X	X	X	X
X			X
X	X	X	X
			1

$$RA = Cx'$$

X	X	1	
X			
X	X	X	X

$$SB = A'B'x$$

X	X		X
	1	1	1
X	X	X	X
X	X	X	X

$$RB = BC + Bx$$

X	X		X
1			X
X	X	X	X
1			X

$$SC = x'$$


X	X	1	
	X	1	
X	X	X	X
	X	1	

$$RC = x$$


X	X		
X	X	X	X
	1	1	

$$y = Ax$$

 Design With Unused States Using SR Flip Flop



Design of Counter

 

Design of Counter

Excitation Table for 3-Bit Counter

Present State			Next State			Flip-Flop Inputs		
A_2	A_1	A_0	A_2	A_1	A_0	TA_2	TA_1	TA_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	1	1
1	1	1	0	0	0	1	1	1

Design of Counter

Handwritten labels: A_2 (row), A_0A_1 (column), A_1 (group), A_0 (group)

	00	01	11	10
0			1	
1			1	

$$TA_2 = A_1 A_0$$

Handwritten labels: A_0A_1 (column), A_1 (row)


	00	01	11	10
0		1	1	
1		1	1	

$$TA_1 = A_0$$

1	1	1	1
1	1	1	1

$$TA_0 = 1$$

Design of Counter

 

Counter for Non-Binary Sequence

Excitation Table for Counter

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

Counter for Non-Binary Sequence

