

Chapter 7

Registers, Counters & the Memory Units

Registers

 


FIGURE 7-1

4-bit register

Register with Parallel Load

 


FIGURE 7-2

4-bit register with parallel load

Register with Parallel Load

 


FIGURE 7-3

Register with parallel load using D flip-flops

Shift Register

 


FIGURE 7-7
Shift register


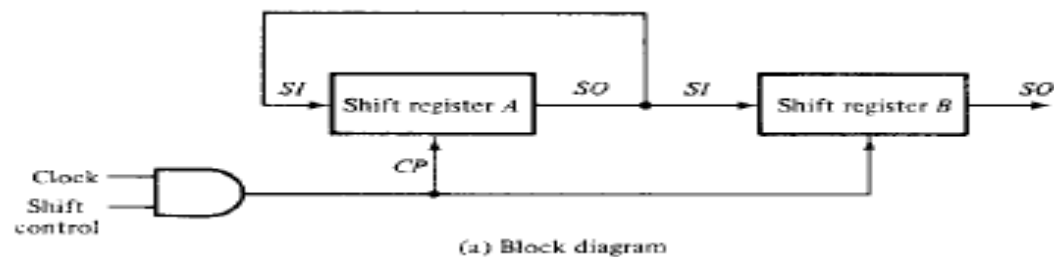



TABLE 7-1
Serial-Transfer Example

Timing Pulse	Shift Register A	Shift Register B	Serial Output of B
Initial value	0 1 1	0 0 1 0	0
After T_1	1 1 0 1	1 0 0 1	1
After T_2	1 1 1 0	1 1 0 0	0
After T_3	0 1 1 1	0 1 1 0	0
After T_4	1 0 1 1	1 0 1 1	1

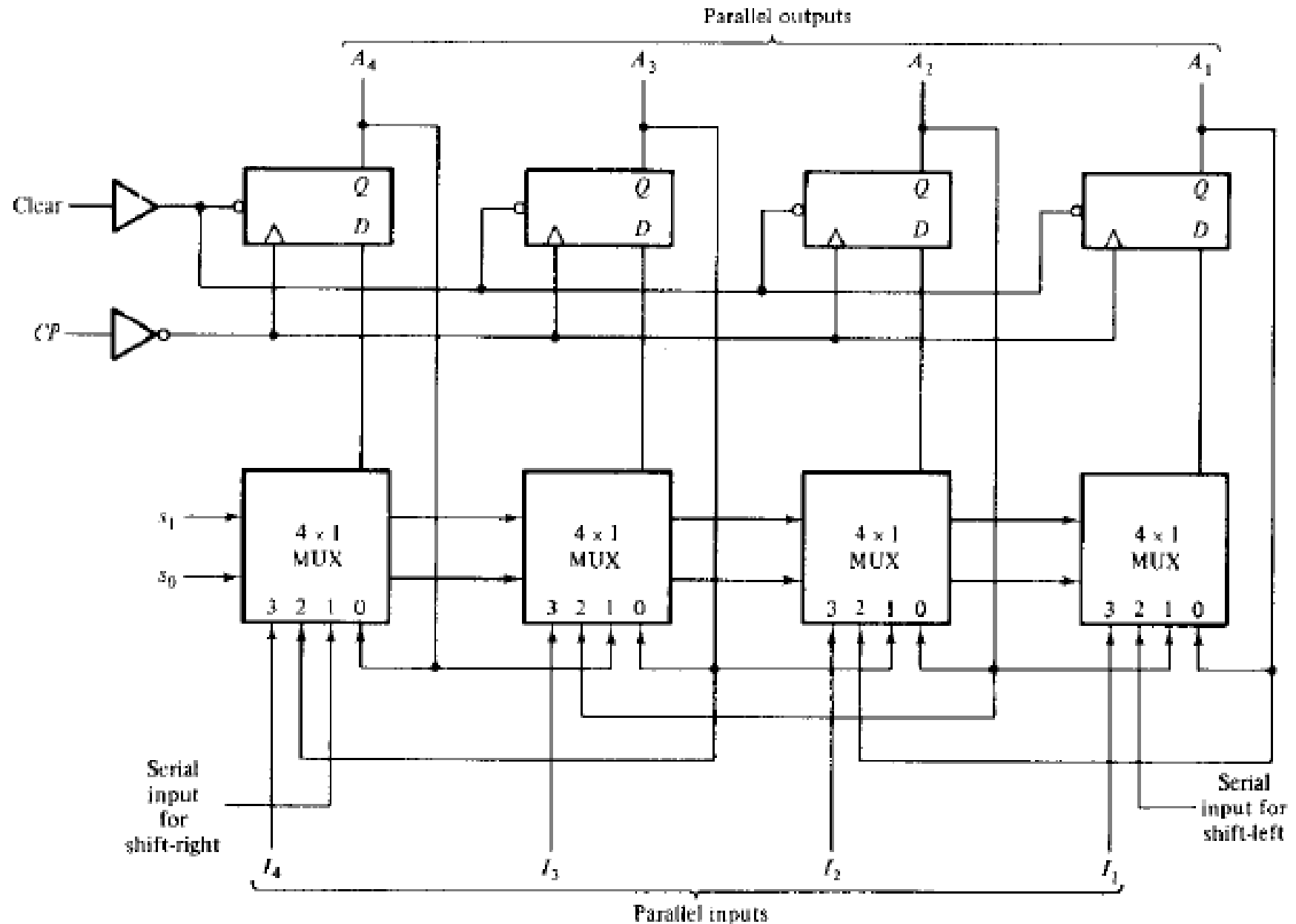4-Bit Bidirectional Shift Register with Parallel Load



4-Bit Binary Ripple Counter

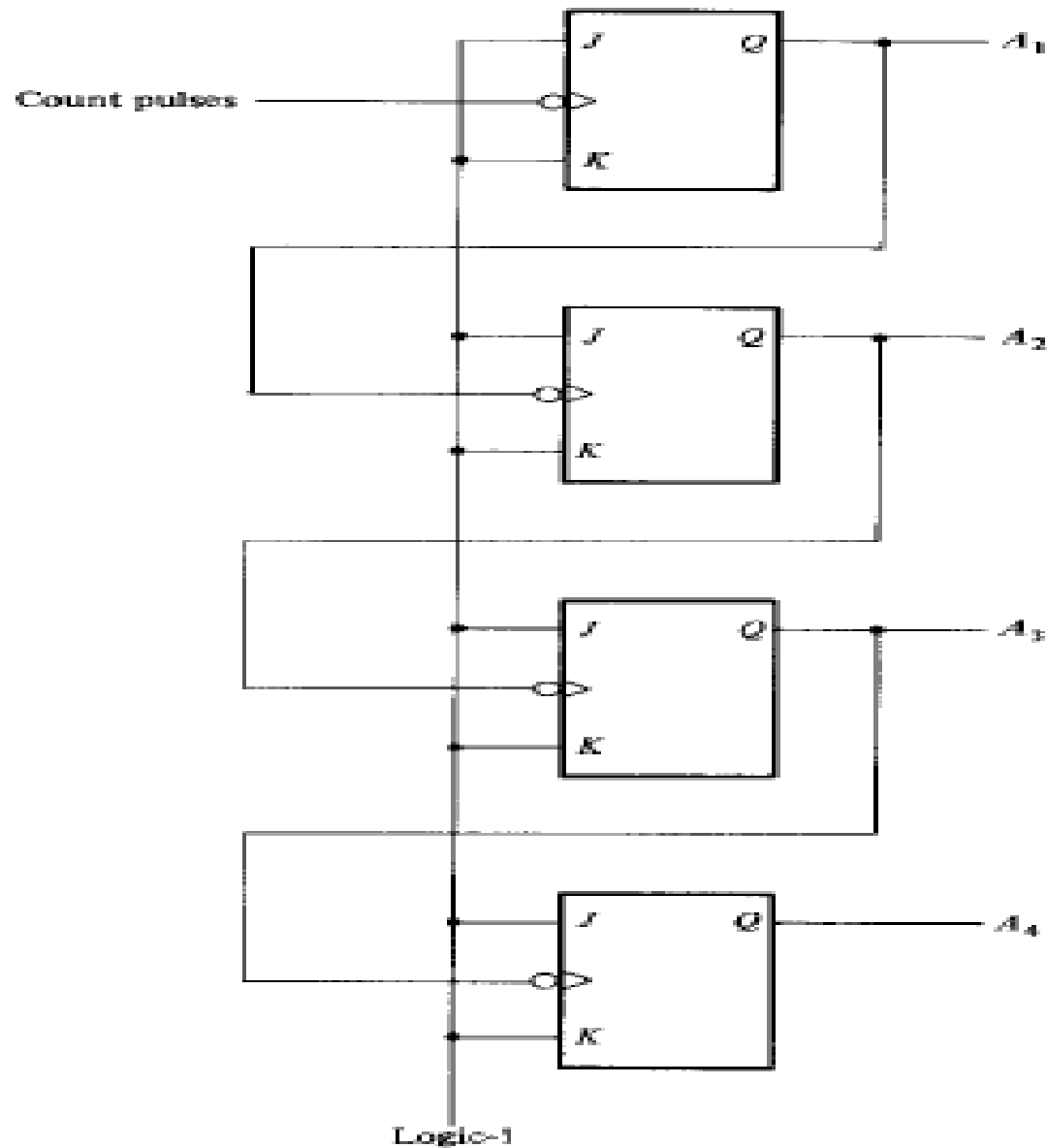

4-Bit Binary Ripple Counter

TABLE 7-4
Count Sequence for a Binary Ripple Counter

Count Sequence				Conditions for Complementing Flip-Flops	
A_4	A_3	A_2	A_1		
0	0	0	0	Complement A_1	
0	0	0	1	Complement A_1	A_1 will go from 1 to 0 and complement A_2
0	0	1	0	Complement A_1	
0	0	1	1	Complement A_1	A_1 will go from 1 to 0 and complement A_2 ; A_2 will go from 1 to 0 and complement A_3
0	1	0	0	Complement A_1	
0	1	0	1	Complement A_1	A_1 will go from 1 to 0 and complement A_2
0	1	1	0	Complement A_1	
0	1	1	1	Complement A_1	A_1 will go from 1 to 0 and complement A_2 ; A_2 will go from 1 to 0 and complement A_3 ; A_3 will go from 1 to 0 and complement A_4
1	0	0	0		
				and so on . . .	

BCD Ripple Counter



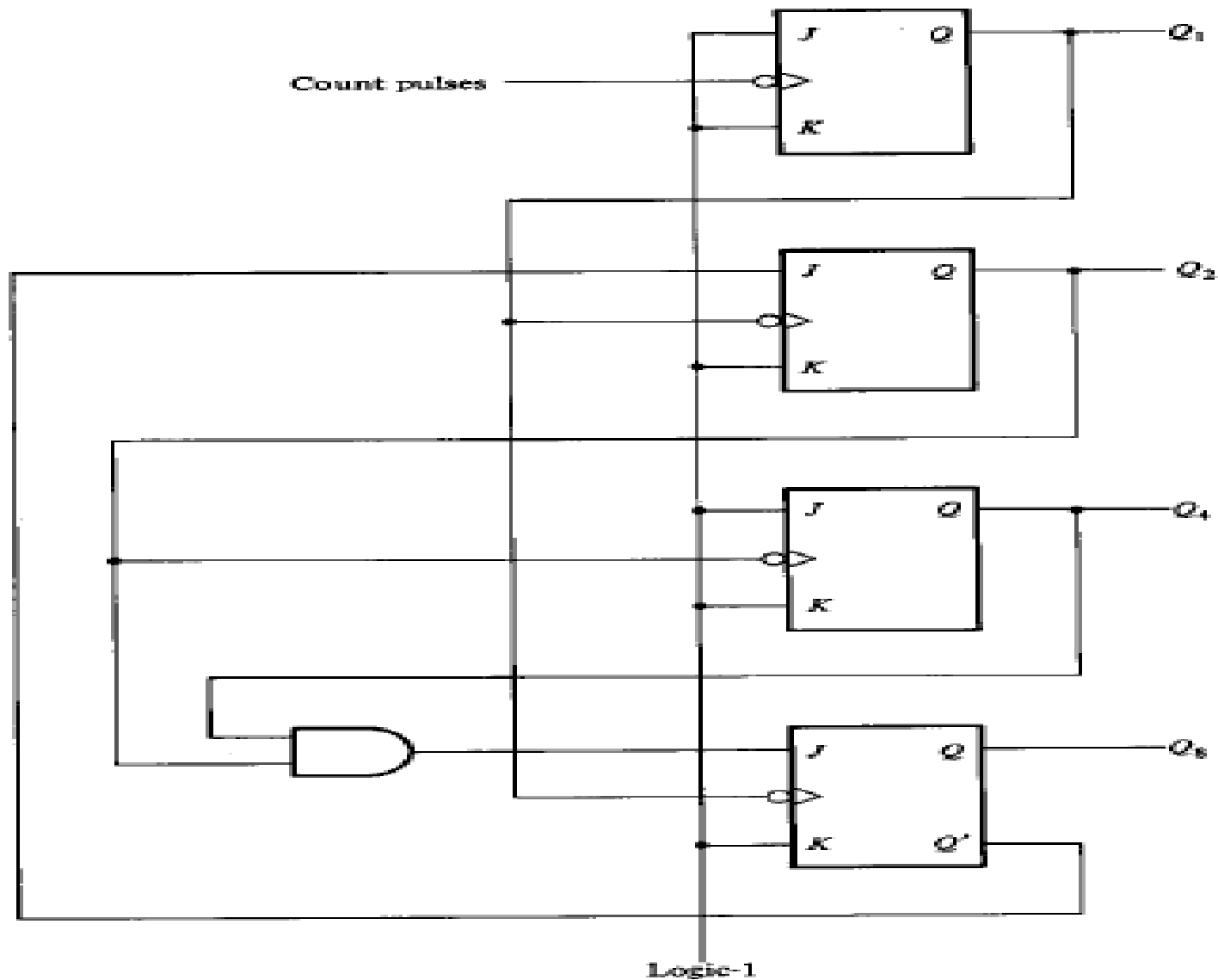


FIGURE 7-14
BCD ripple counter


4 Bit Synchronous Binary Counter

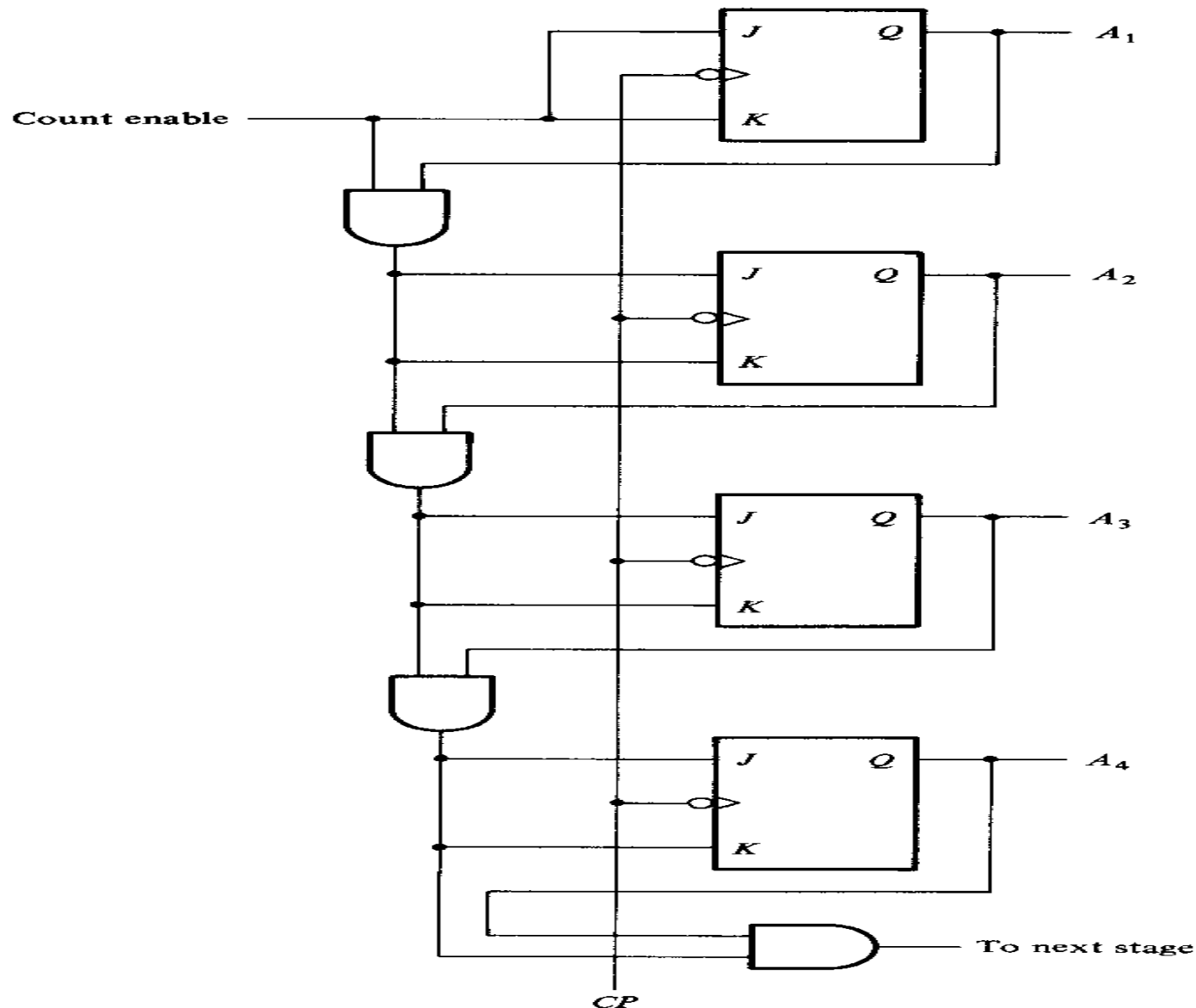

4 Bit Binary Up Down Counter

 

Johnson Counter

 

(a) Four-stage switch-tail ring counter


Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	AB'
3	1	1	0	0	BC'
4	1	1	1	0	CE'
5	1	1	1	1	AE
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

(b) Count sequence and required decoding.


FIGURE 7-23

Construction of a Johnson counter

Memory Cell (Binary Cell)

 

(a) Logic diagram

 

(b) Block diagram

FIGURE 7-26
Memory cell

Logical Construction of RAM (4 X 3)

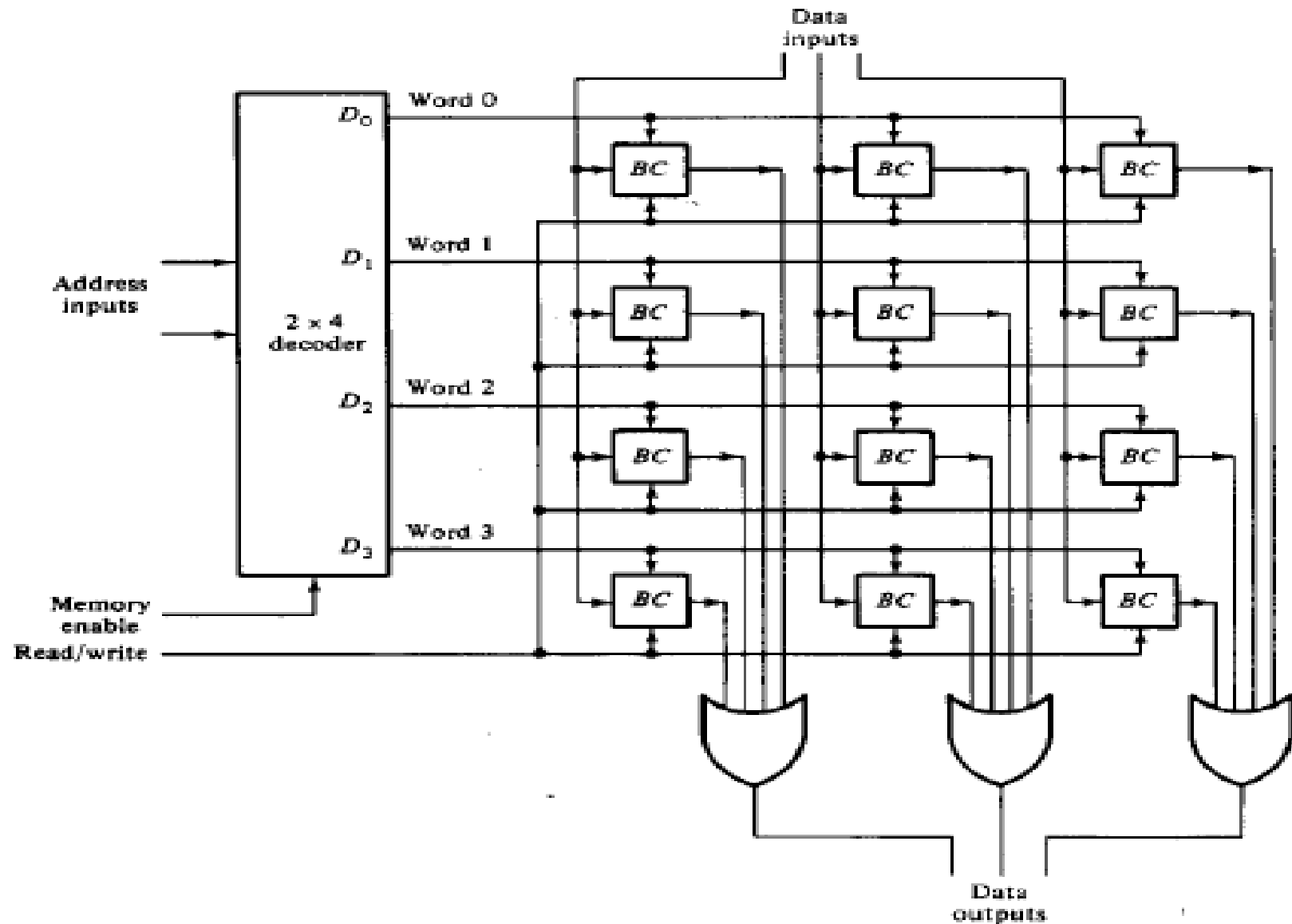


FIGURE 7-27
Logical construction of a 4 X 3 RAM

1K X 8 RAM


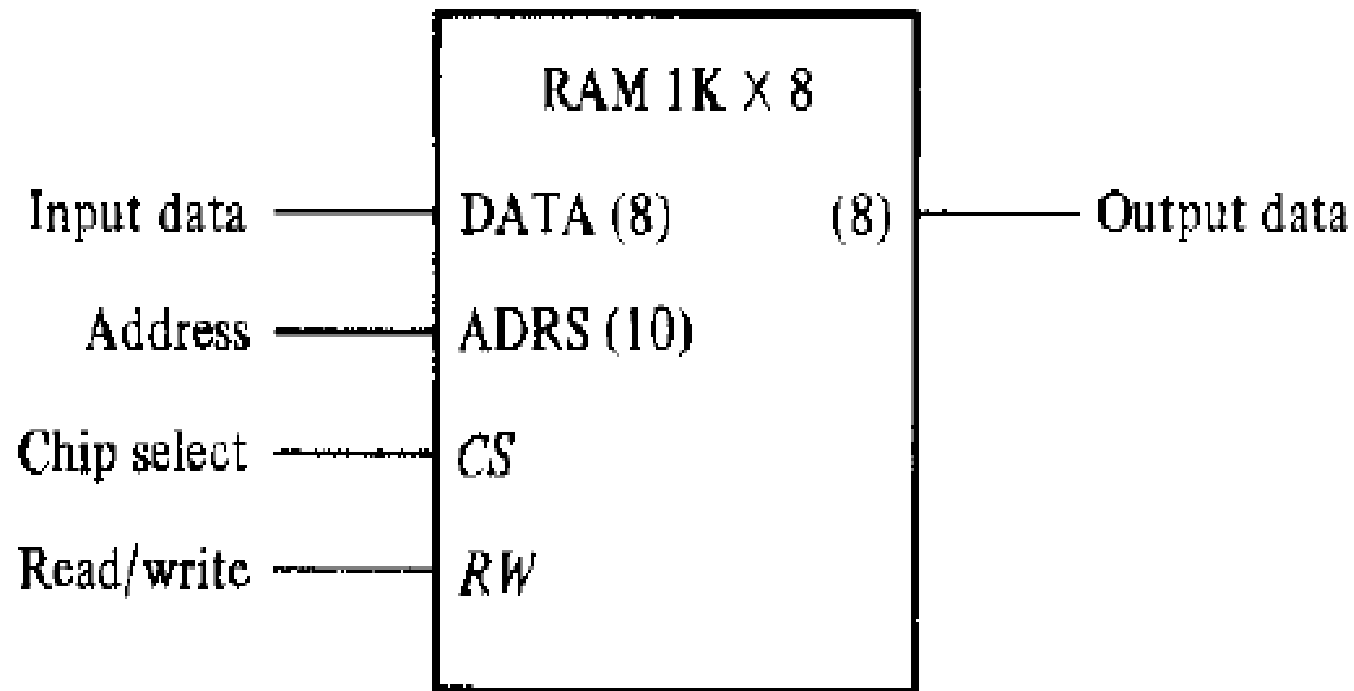


FIGURE 7-28

Block diagram of a 1K \times 8 RAM chip.

4K X 8 RAM

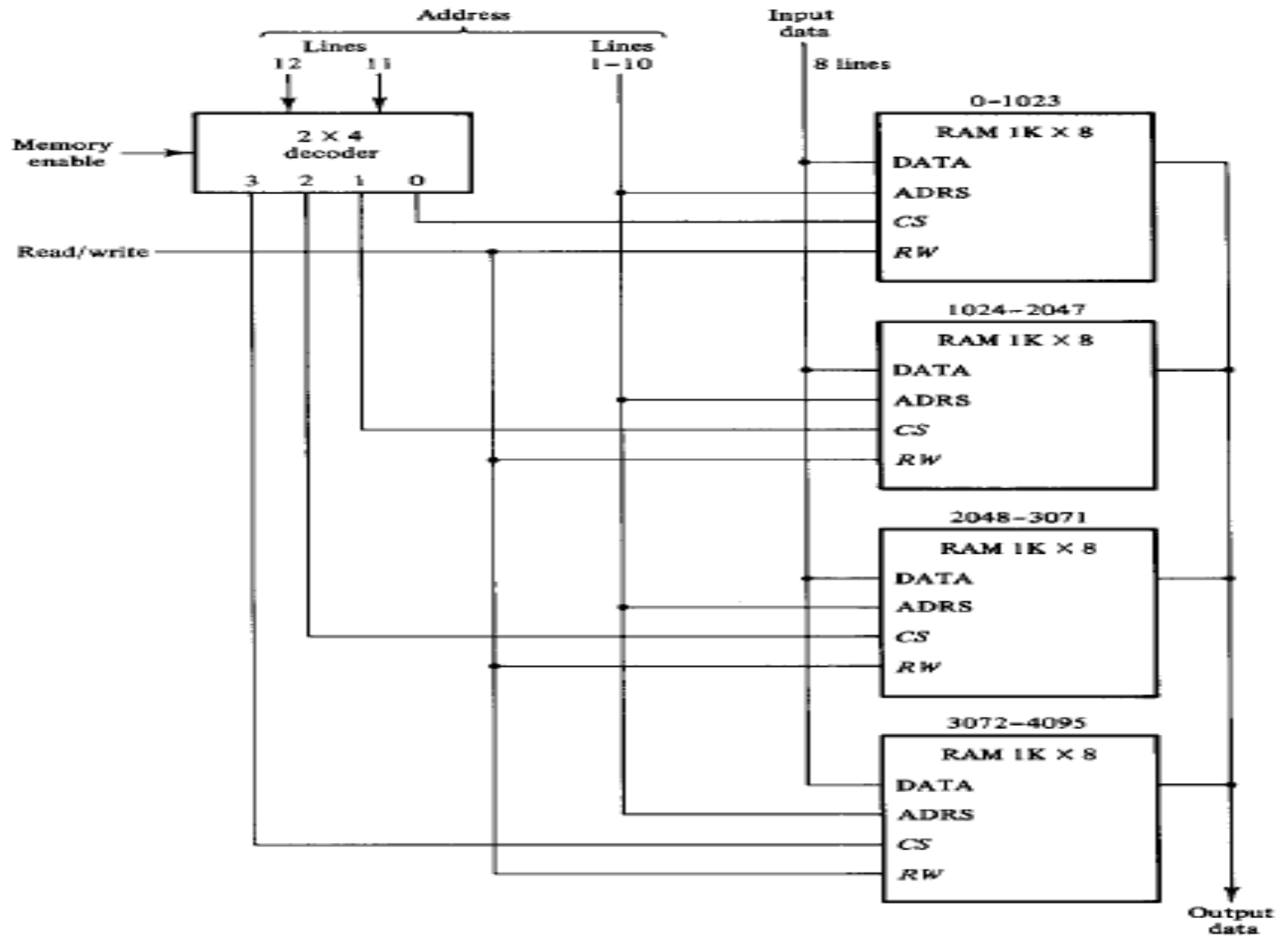

1K X 16 RAM

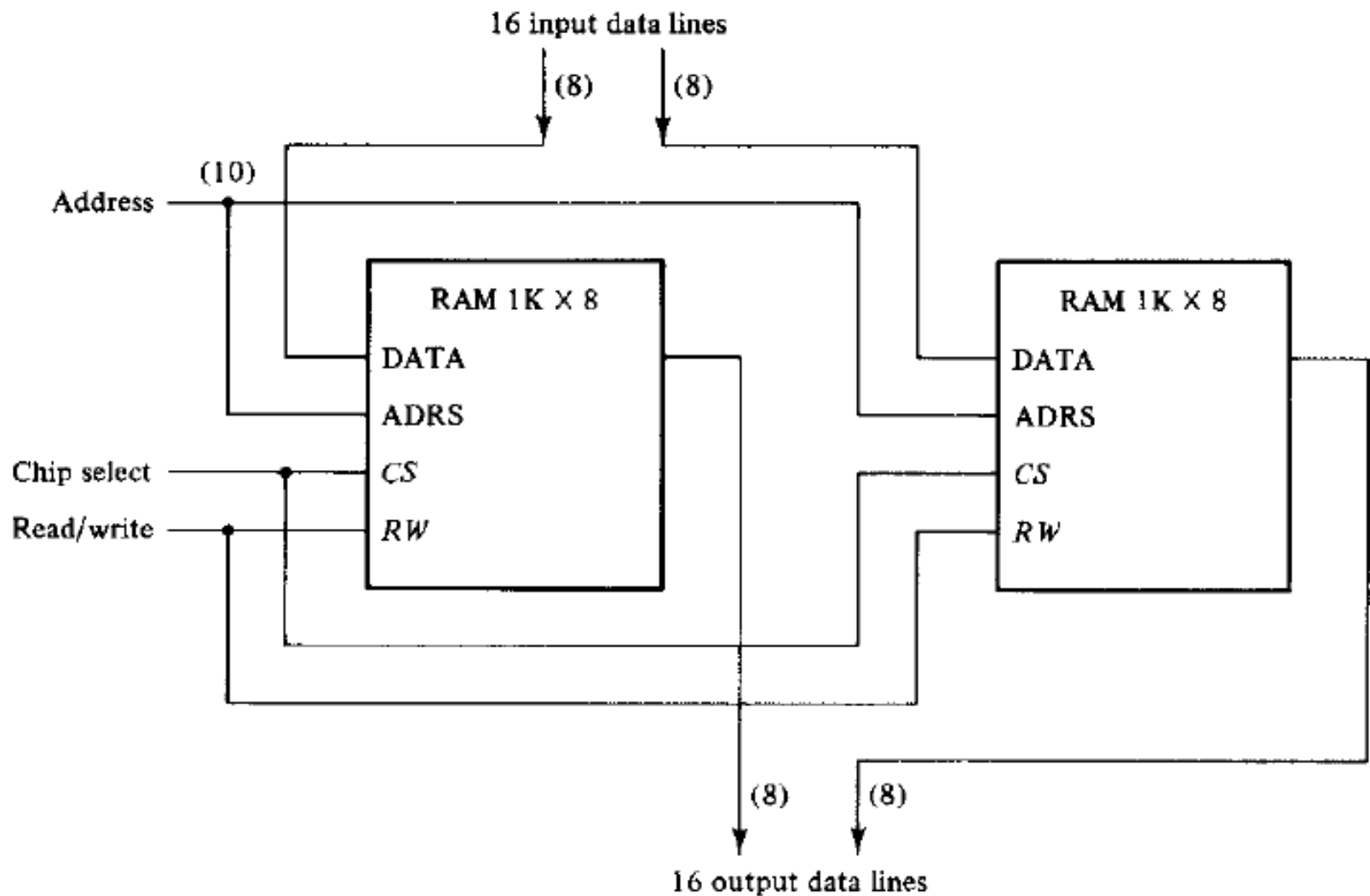


FIGURE 7-30

Block diagram of a 1K X 16 RAM.