

## ASSIGNMENT-1

1. Use mesh analysis to find the current in each resistor in Fig. 3.15.

[in  $100\ \Omega = 0.1\text{ A}$  from  $L$  to  $R$  ; in  $20\ \Omega = 0.4\text{ A}$  from  $R$  to  $L$  ; in  $10\ \Omega = 0.5\text{ A}$  downward]

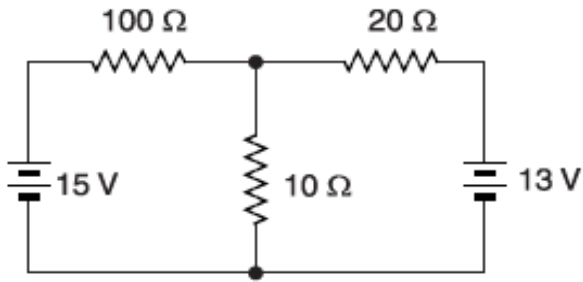


Fig. 3.15

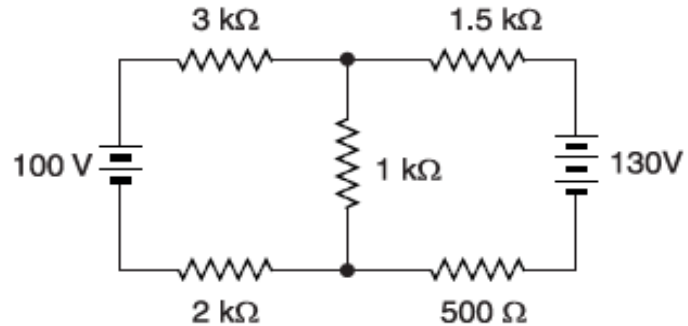


Fig. 3.16

2. Using mesh analysis, find the voltage drop across the  $1\text{ k}\Omega$  resistor in Fig. 3.16. [50 V]

3. Using mesh analysis, find the currents in  $50\ \Omega$ ,  $250\ \Omega$  and  $100\ \Omega$  resistors in the circuit shown in Fig. 3.17.  
[ $I(50\ \Omega) = 0.171\text{ A} \rightarrow$  ;  $I(250\ \Omega) = 0.237\text{ A} \leftarrow$  ;  $I(100\ \Omega) = 0.408\text{ A} \downarrow$ ]

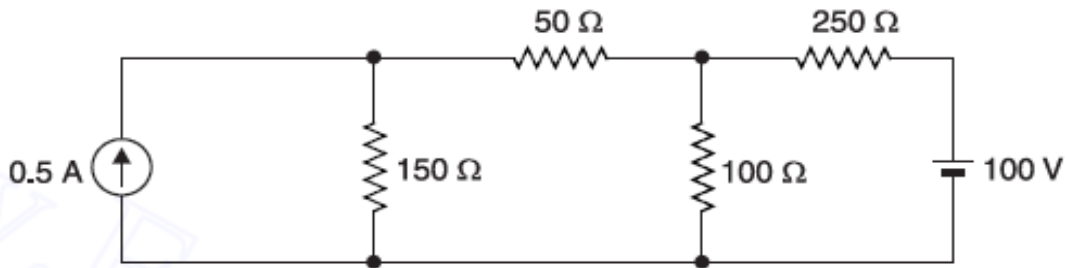


Fig. 3.17

4. For the network shown in Fig. 3.18, find the mesh currents  $I_1$ ,  $I_2$  and  $I_3$ . [5 A, 1 A, 0.5 A]

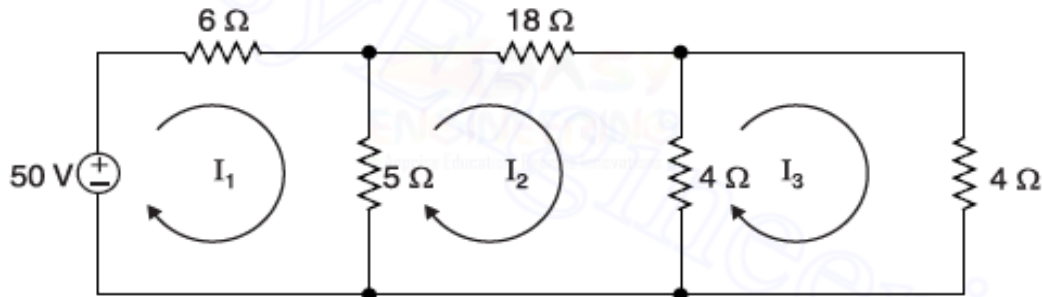


Fig. 3.18

5. In the network shown in Fig. 3.19, find the magnitude and direction of current in the various branches by mesh current method.  
[ $FAB = 4\text{ A}$  ;  $BF = 3\text{ A}$  ;  $BC = 1\text{ A}$  ;  $EC = 2\text{ A}$  ;  $CDE = 3\text{ A}$ ]

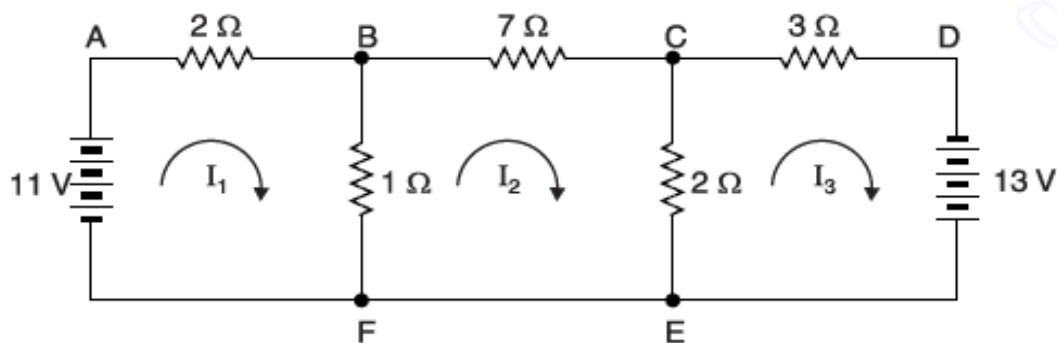


Fig. 3.19

## ASSIGNMENT:2

1. Using nodal analysis, find the voltages at nodes  $A$ ,  $B$  and  $C$  w.r.t. the reference node shown by the ground symbol in Fig. 3.39.

$[V_A = -30\text{V} ; V_B = -20\text{V} ; V_C = -2\text{V}]$

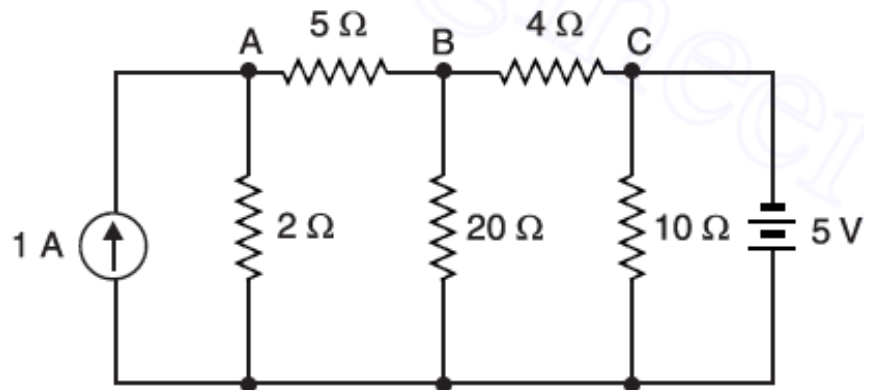
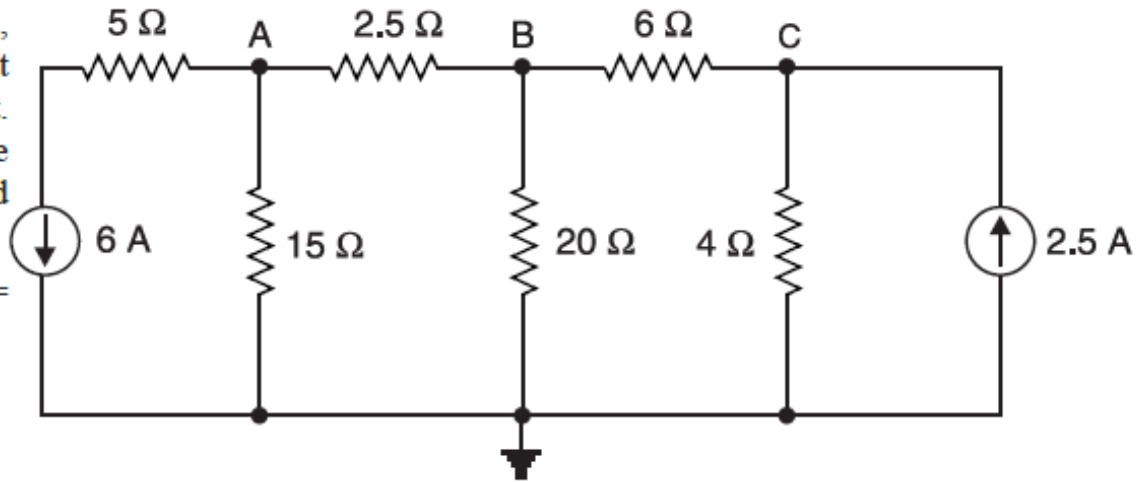


Fig. 3.44

2. Find Node Voltage In Figure 3.44. (Ans.  $V_A = 0.806\text{ V}$ ,  $V_B = -2.18\text{ V}$ ,  $V_C = -2.5\text{ V}$ )
3. Using nodal analysis find the current through the battery In Figure 3.44. (Ans.  $1.21\text{ A}$ )

### Assignment-3

1. For the circuit shown in Fig.1 below calculate the current taken by circuit.

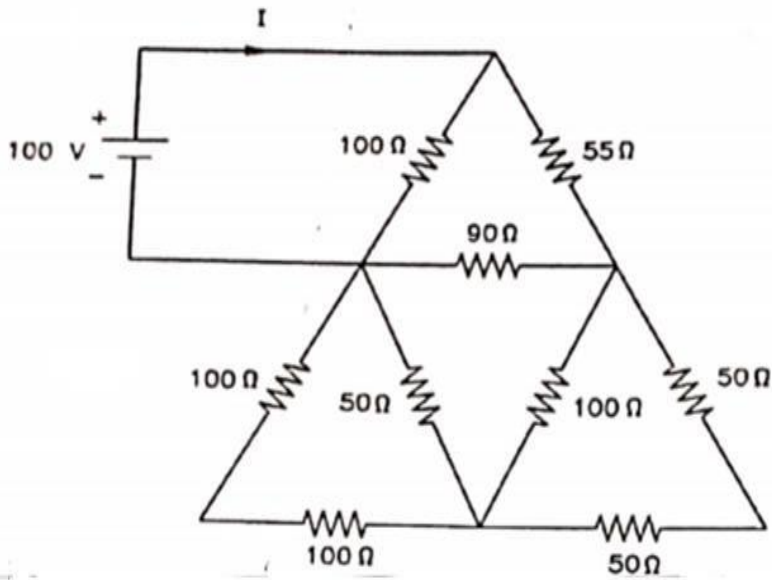


Fig.1

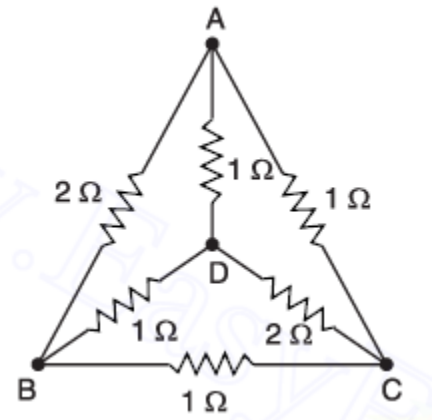


Fig.2

2. In the network shown in Fig.2, find the resistance between terminals B and C using star/delta transformation.
3. Find the current supplied by the battery in the network shown in Fig.3.

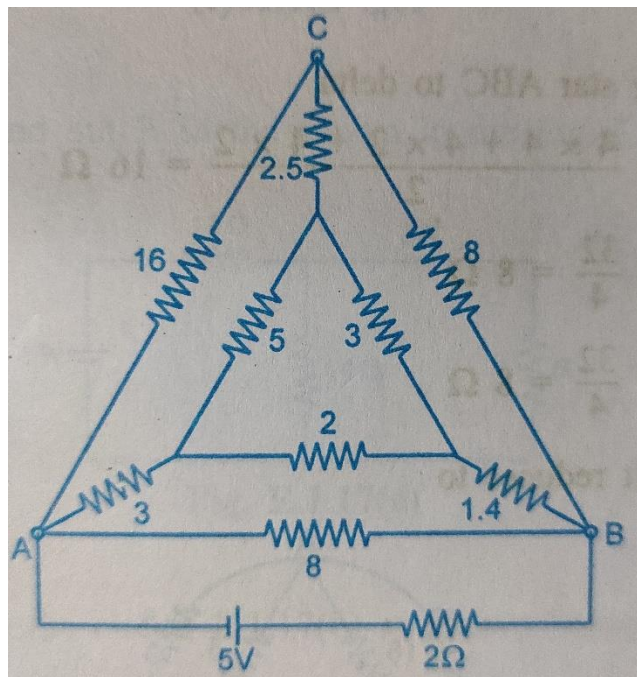


Fig.3.

## Assignment-4

**Q.1** Two series connected parallel plate capacitors have plate areas of  $0.2 \text{ m}^2$  and  $0.04 \text{ m}^2$ , plate separation of  $0.5 \text{ mm}$  and  $0.125 \text{ mm}$  and relative permittivities of  $1$  and  $6$  respectively. Calculate the total voltage across the capacitors that will produce a potential gradient of  $100 \text{ kV/cm}$  between the plates of first capacitor.

Ans.  $V=6.04 \text{ Kv}$

**Q.2.** A capacitor is composed of two plates separated by  $3 \text{ mm}$  of dielectric of permittivity  $4$ . An additional piece of insulation  $5 \text{ mm}$  thick is now inserted between the plates. If the capacitor now has capacitance one-third of its original capacitance, find the relative permittivity of the additional dielectric.

Ans.  $\therefore \epsilon_{r2} = 20/6 = 3.33$

- 3 A capacitor is being charged from a d.c. source through a resistance of  $2 \text{ M}\Omega$ . If it takes  $0.2$  second for the charge to reach  $75\%$  of its final value, what is the capacitance of the capacitor ? Ans.  $16.67 \times 10^{-4} \text{ F}$
- 4 A  $8 \mu\text{F}$  capacitor is connected in series with  $0.5 \text{ M}\Omega$  resistance across  $200 \text{ V}$  supply. Calculate (i) initial charging current (ii) the current and p.d. across capacitor  $4$  seconds after it is connected to the supply.  
[(i)  $400 \mu\text{A}$  (ii)  $147 \mu\text{A}$ ;  $126.4 \text{ V}$ ]
- 5 What resistance connected in series with a capacitance of  $4 \mu\text{F}$  will give the circuit a time constant of  $2$  seconds ?  
[ $500 \text{ k}\Omega$ ]
- 6 A series  $RC$  circuit is to have an initial charging current of  $4 \text{ mA}$  and a time constant of  $3.6$  seconds when connected to  $120 \text{ V}$  d.c. supply. Calculate the values of  $R$  and  $C$ . What will be the energy stored in the capacitor ?  
[ $30 \text{ k}\Omega$  ;  $120 \mu\text{F}$  ;  $0.864 \text{ J}$ ]
- 7 A  $20 \mu\text{F}$  capacitor initially charged to a p.d. of  $500 \text{ V}$  is discharged through an unknown resistance. After one minute, the p.d. at the terminals of the capacitor is  $200 \text{ V}$ . What is the value of the resistance ?  
[ $3.274 \text{ M}\Omega$ ]

## Assignment-5

**Q.1** A ring has mean diameter of 15 cm, a cross-section of  $1.7 \text{ cm}^2$  and has a radial gap of 0.5 mm cut in it. It is uniformly wound with 1500 turns of insulated wire and a current of 1 A produces a flux of 0.1 mWb across the air gap. Calculate the relative permeability of iron on the assumption that there is no magnetic leakage.

**Ans. Relative permeability=174**

**Q.2** The self inductance of a coil of 500 turns is 0.25 H. If 60% of the flux is linked with a second coil of 10500 turns, calculate :-

- (i) the mutual inductance between the coils and
- (ii) e.m.f. induced in the second coil when current in the first coil changes at the rate of 100 A/sec

**Ans. 1).  $M=3.15 \text{ H}$**

**2).  $E= 315 \text{ V}$**



## ASSIGNMENT-6

1. An alternating voltage is represented by :

$$v = 141.4 \sin 377 t$$

Find (i) the maximum value (ii) frequency (iii) time period and (iv) the instantaneous value of voltage when  $t$  is 3 ms.  
[(i) 141.4V (ii) 60 Hz (iii) 16.67 ms (iv) 127.8 V]

2. An alternating current of frequency 50Hz has a maximum value of  $200\sqrt{2}$ A. Reckoning the time from the instant the current is zero and becoming positive, find the time taken by the current to reach a value of 141.4A for a first and second time. [1.67 ms ; 21.67 ms]
3. An alternating current takes 3.375 ms to reach 15 A for the first time after becoming instantaneously zero. The frequency of current is 40 Hz. Find the maximum value of alternating current. [20A]
4. A 50 Hz sinusoidal voltage has a maximum value of 56.56 V. Find the value of voltage 0.0025 second after passing through maximum positive value. At what time measured from a positive maximum value will instantaneous voltage be 14.14 V ? [40V ; 4.2 ms]
5. An alternating current of frequency 50 Hz has a maximum value of 100A. Calculate its value 1/300 second after the instant the current is zero and its value is decreasing thereafter. [-86.6 A]

## ASSIGNMENT-7

1. Determine the inductance required to series-resonate with a 180 pF capacitor at 320 kHz. Also determine  $BW$  and  $Q$  if  $R = 20 \Omega$ .  
[ $L = 1.373 \text{ mH}$ ;  $BW = 2.32 \text{ kHz}$ ;  $Q = 138$ ]
2. A series  $LC$  circuit has an inductance of 200  $\mu\text{H}$ , a capacitance of 300 pF and a  $Q$  of 60. Determine  $f_r$ ,  $BW$  and upper and lower cut-off frequencies.  
[ $f_r = 649.75 \text{ kHz}$ ;  $BW = 10.83 \text{ kHz}$ ; 655.16 kHz; 644.34 kHz]
3. A resistance of 15  $\Omega$  and an inductance of 4H and a capacitance of 25  $\mu\text{F}$  are connected in series across 230 V a.c. supply. Calculate (i) the frequency at which the current shall be maximum (ii) current at this frequency and (iii) p.d. across inductance.  
[(i) 15.9 Hz (ii) 15.33 A (iii) 6123 V]
4. A circuit consists of a resistance of 12  $\Omega$ , capacitance of 320  $\mu\text{F}$  and an inductance of 0.08 H, all in series. A supply of 240 V, 50 Hz is applied to the ends of the circuit. Calculate the frequency at which the circuit power factor would be unity.  
[32 Hz]

## ASSIGNMENT-8

**1.** *Three coils, each having a resistance of  $20\ \Omega$  and an inductive reactance of  $15\ \Omega$ , are connected in star to a  $400\text{ V}$ , 3-phase,  $50\text{ Hz}$  supply. Calculate (i) the line current (ii) power factor and (iii) power supplied.*

**2.** *A 3-phase,  $400\text{ V}$ ,  $50\text{ Hz}$  a.c. supply is feeding a 3-phase delta-connected load with each phase having a resistance of  $25\ \Omega$ , an inductance of  $0.15\text{ H}$  and a capacitor of  $120\ \mu\text{F}$  in series. Find line current, volt-amp, active power and reactive volt-amp.*